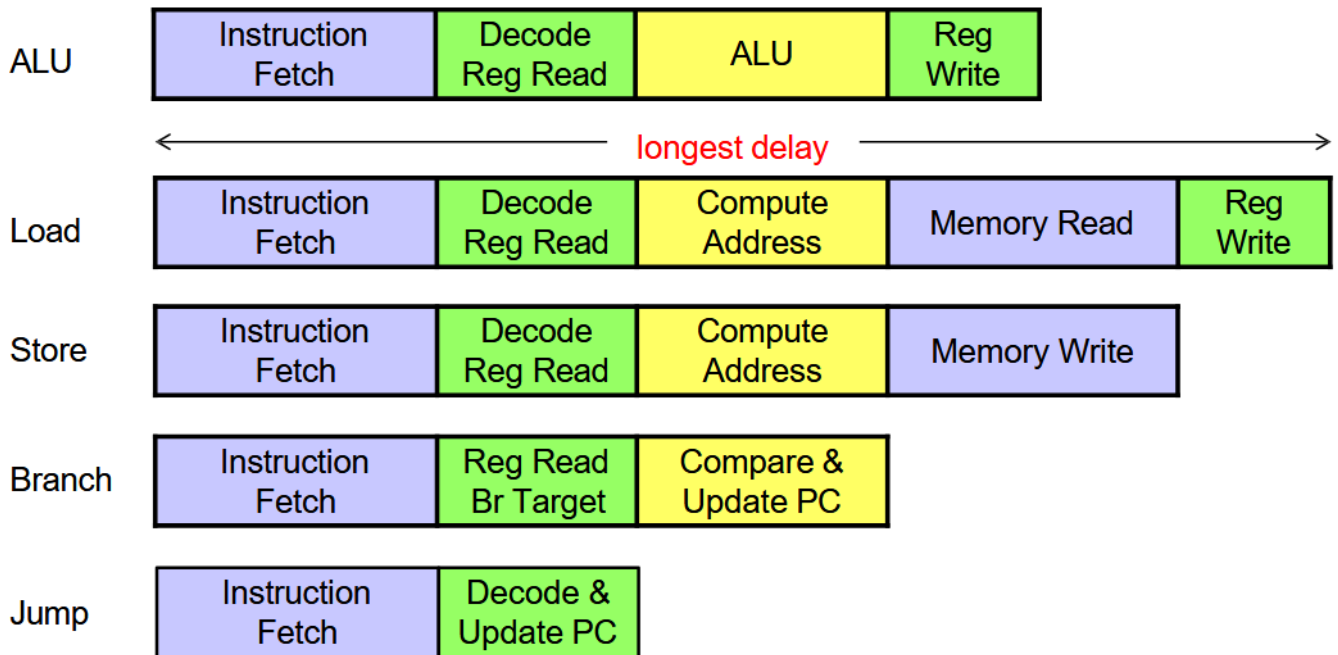


# CSE301 – Computer Organization

## Lecture 4 – Single-Cycle Processor

### Instruction Stages

Each instruction passes through the following stages:




### Single-Cycle Processor


- Executes **each instruction in one clock cycle**.
- The **clock period** must be long enough to accommodate the **slowest instruction**.
- **Drawback:** Overall performance is limited by the slowest instruction.

### Building the Datapath


#### 1. Instruction Fetch

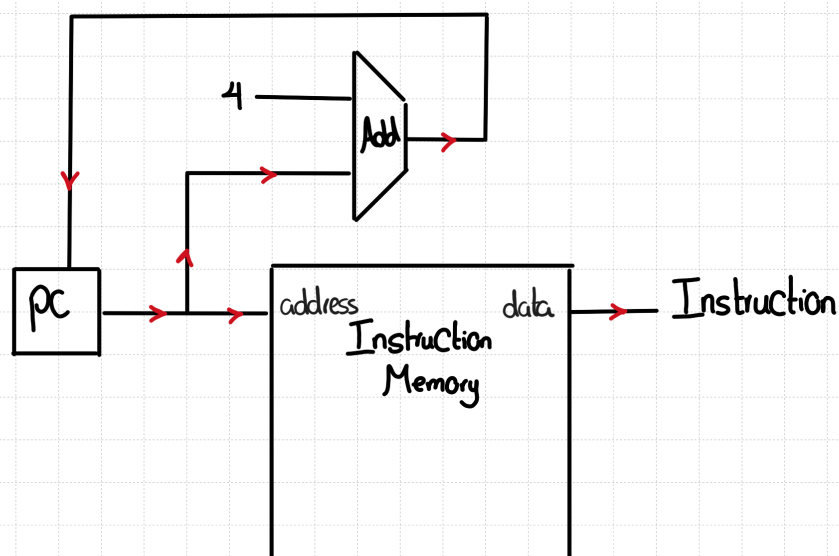


## 2. Adding R-Type Instructions

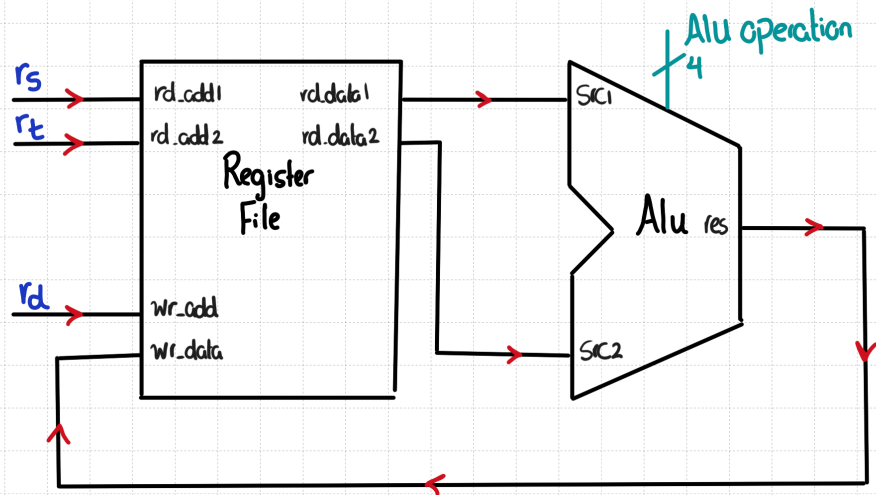

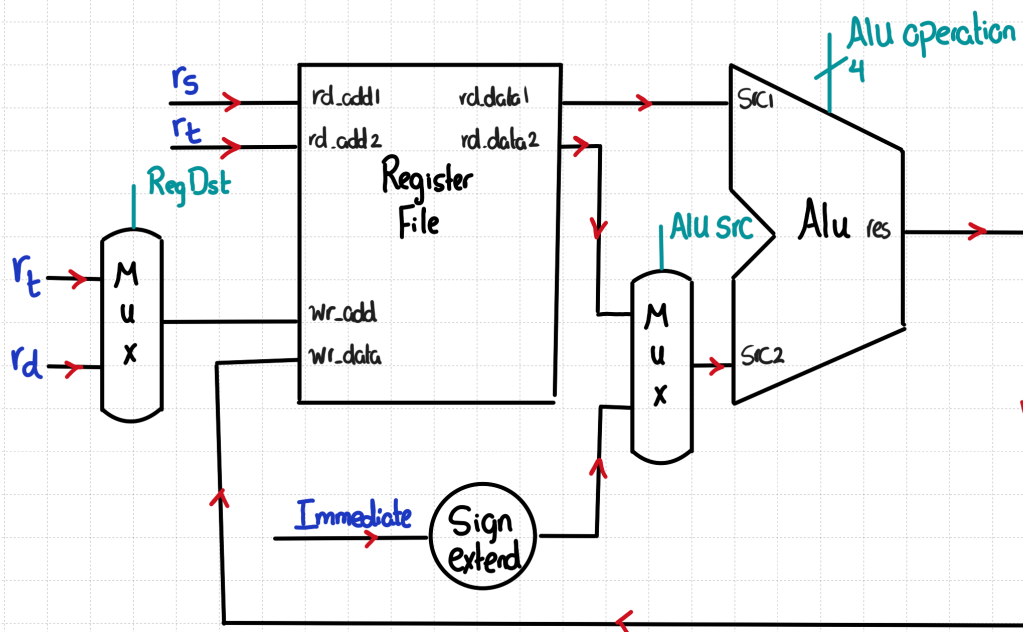
## 3. Adding I-Type Instructions (ALU Operations)



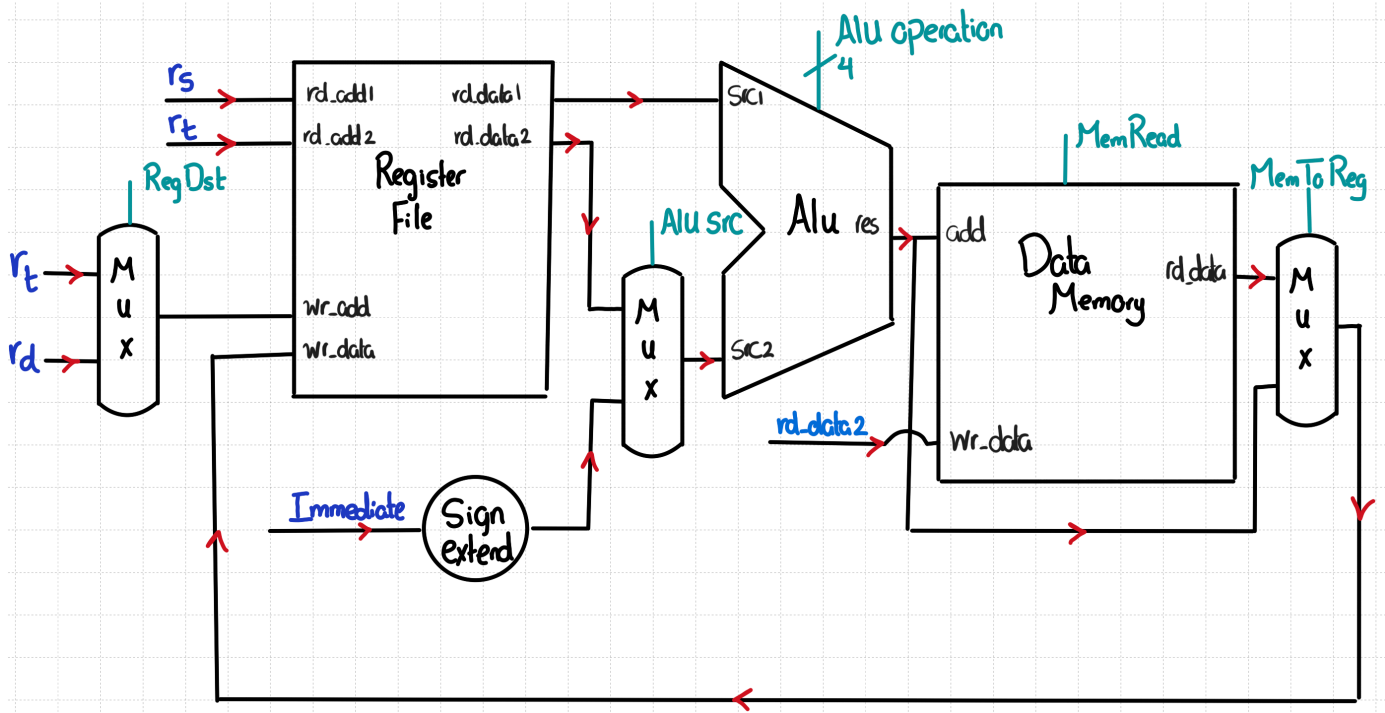
## 4. Adding I-Type Instructions (Load & Store)



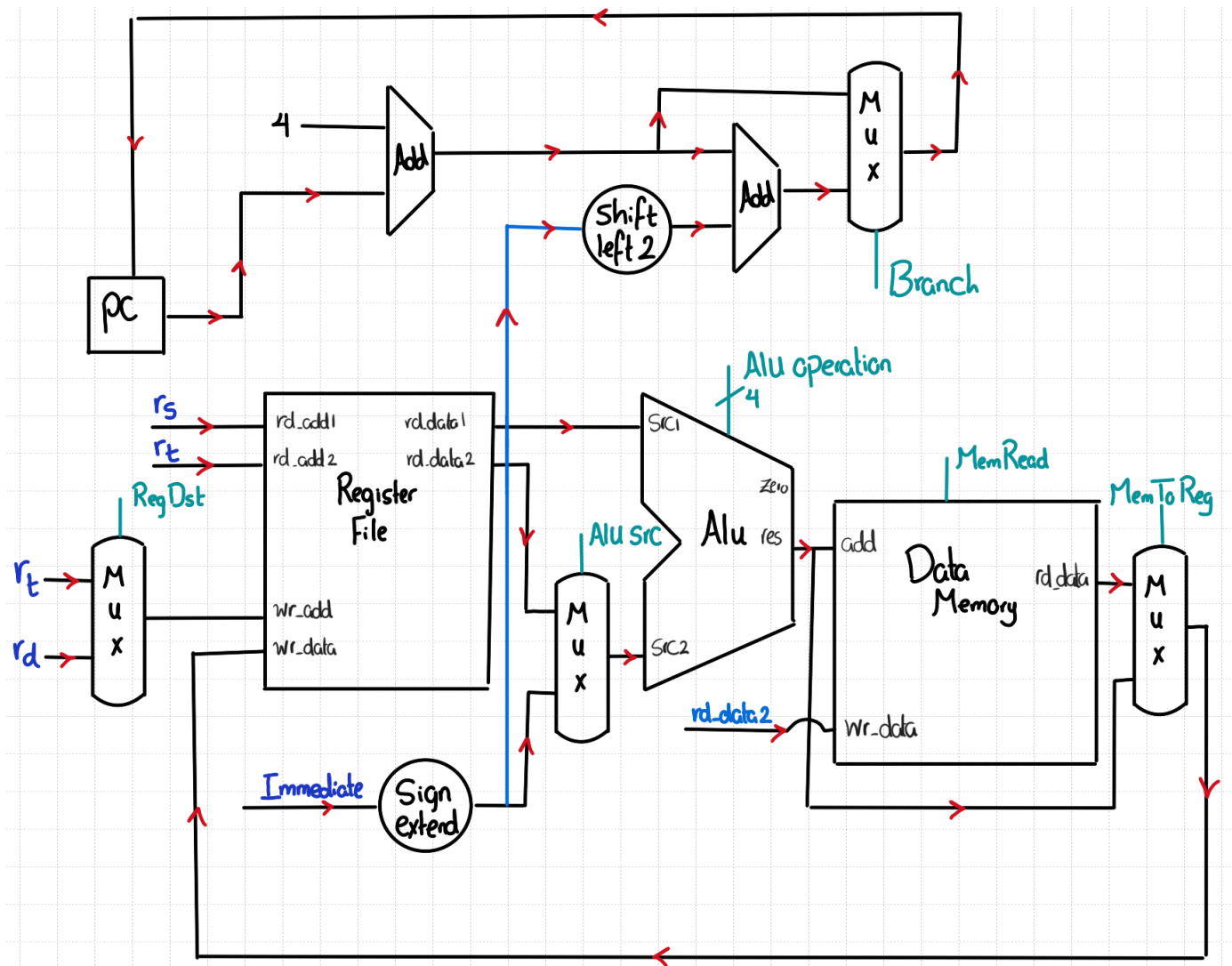
### 5. Adding I-Type Instructions (Branch)



### 6. Adding J-Type Instructions

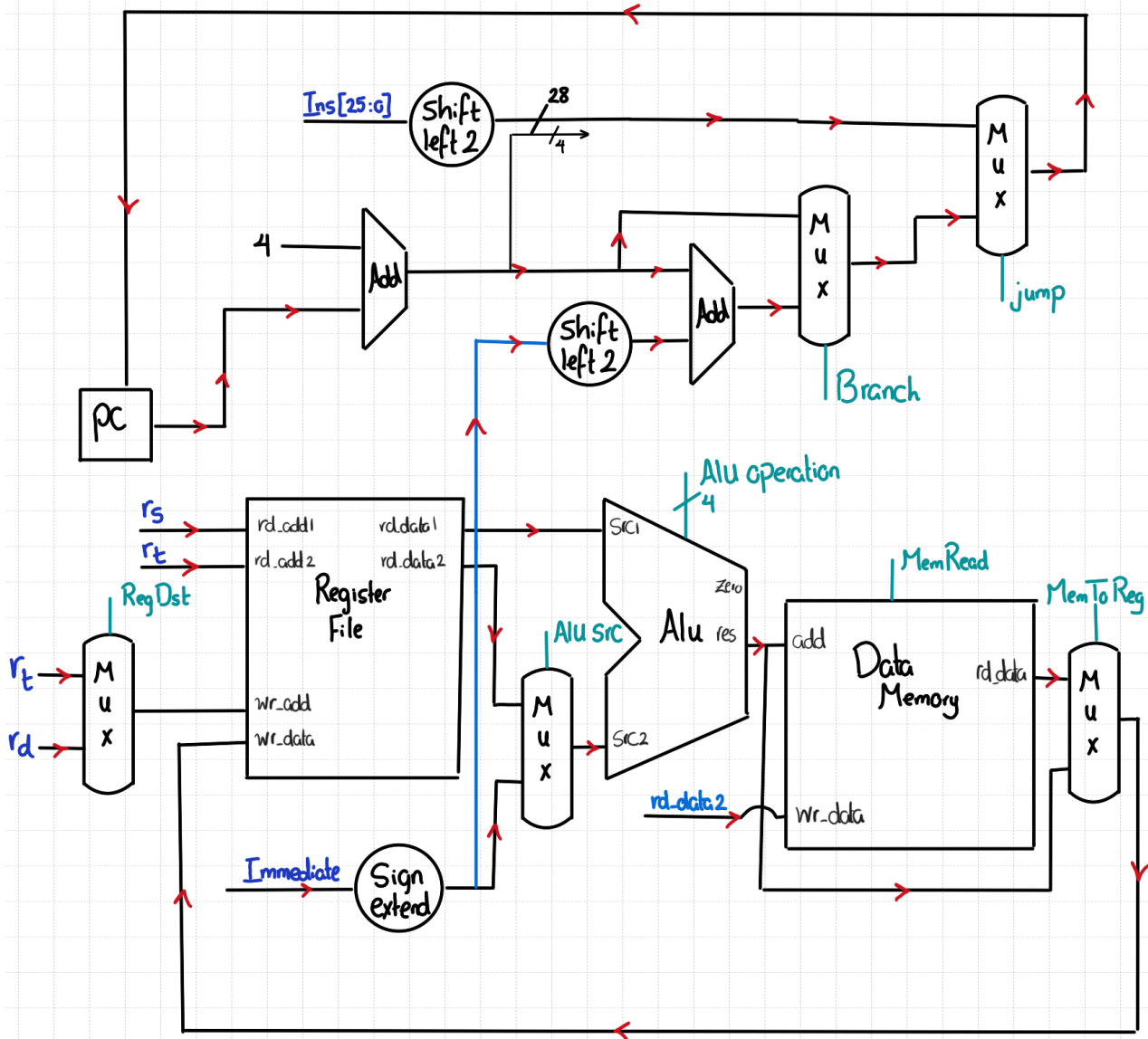

## Control Unit

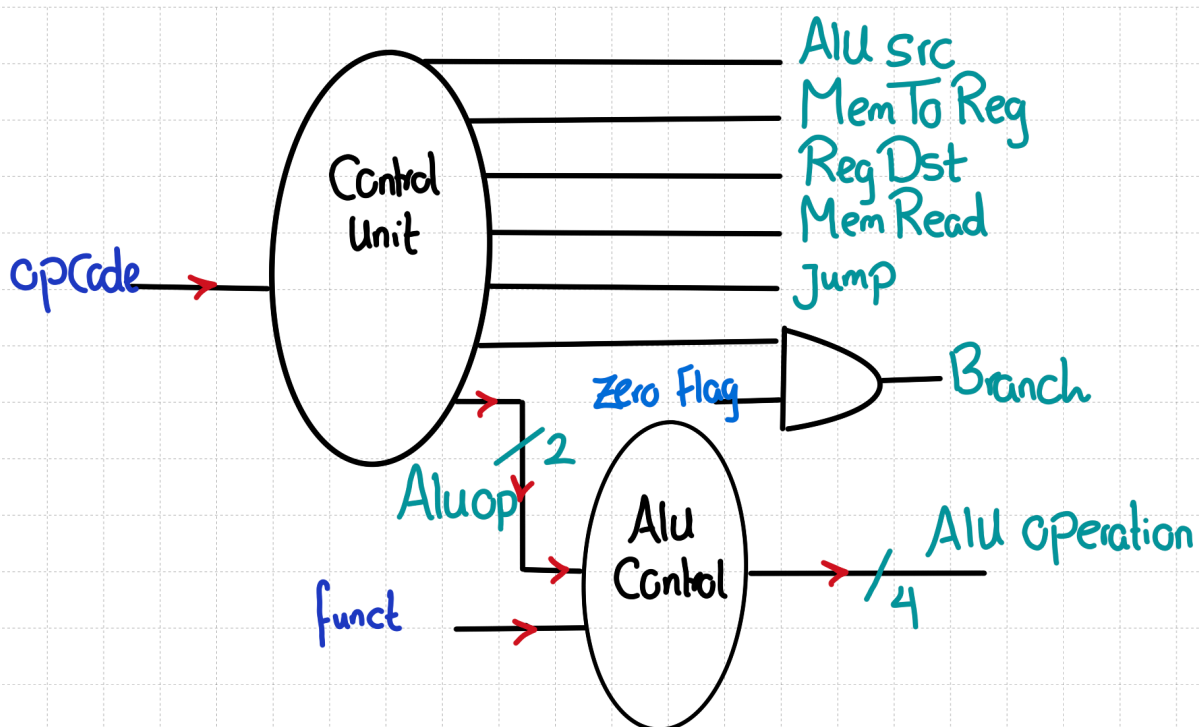

## Performance Considerations

- The **clock period** is determined by the **longest instruction delay**.
- The **critical path** typically occurs in **load instructions**:

Instruction memory → Register file → ALU → Data memory → Register file

- It's **impractical** to change the clock period per instruction.
- Violates the design principle:

"Make the common case fast."